



Digital IC Design


Week3: Gate Level Modeling 1(Basic Overview)

2024 | Nineplus Infotech X Anseong Polytechnic University
Sr Research Engineer, William Woo




1. Gate Level Modeling

Abstraction Level

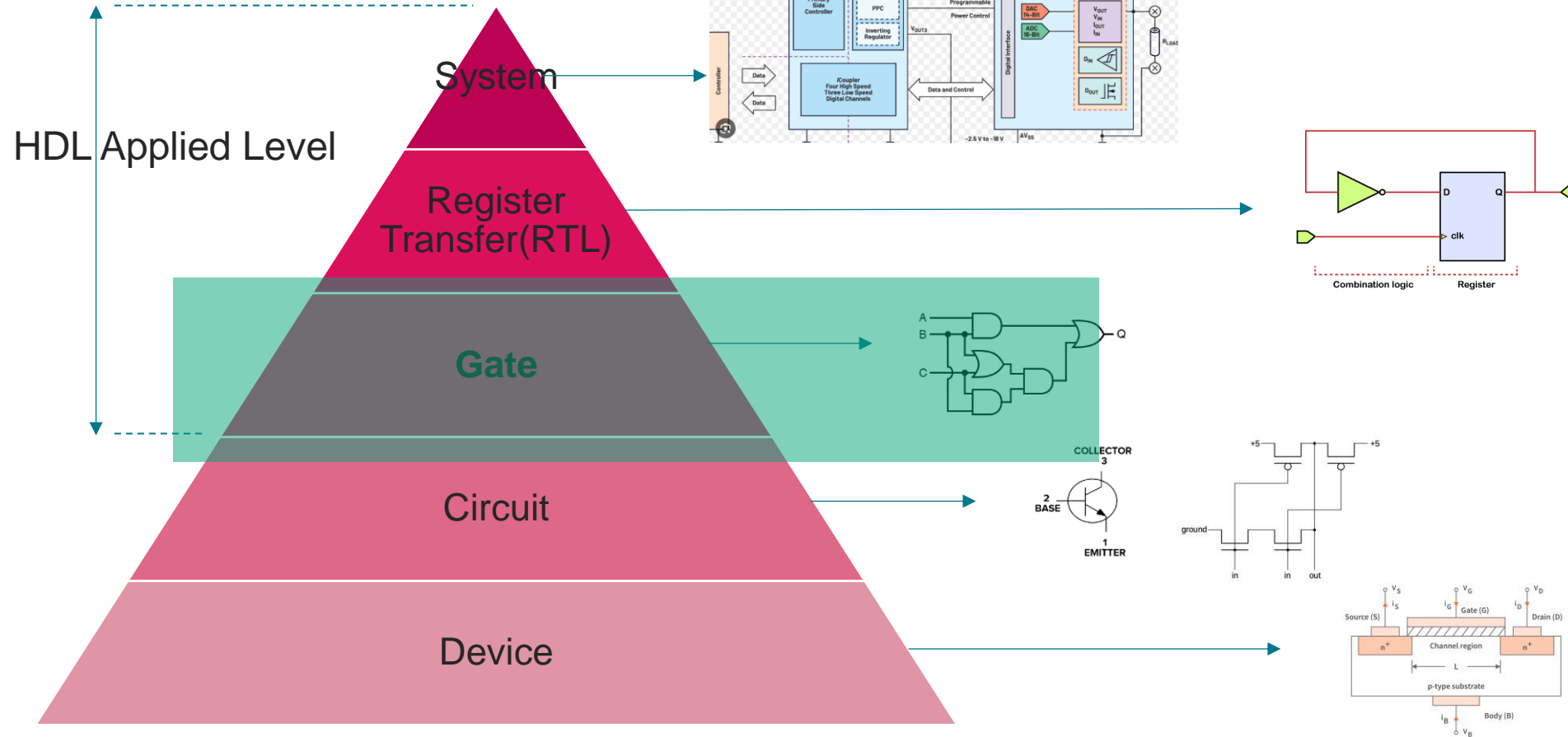

Gate-level Modeling

 

=

◆ Gate-level modeling

- ◆ 게이트 및 연결관계를 직관적으로 표현
- ◆ Gate Schematic과 HDL module이 1:1로 대응

```
1
2 module full_adder_gatelevel_module (a, b, cin, sum, cout);
3     input a, b, cin;
4     output sum, cout;
5
6     // xor_out_1 and xnor_out_2 is not used
7     // wire xor_out_1;
8     wire xnor_out_1;
9     // xnor_out_2;
10    // wire not_out_1;
11
12    wire and_out_1, and_out_2, and_out_3;
13    wire or_out_1;
14
15    //sum = (a⊙b)⊙(cin)
16    //Fill this out
17    xnor_gatelevel_gate xnor_1 (.a(a), .b(b), .out(xnor_out_1));
18    xnor_gatelevel_gate xnor_2 (.a(xnor_out_1), .b(cin), .out(sum));
19
20    //cout = b(cin) + a(cin) + ab
21    //Fill this out
22    and_gate and_1 (.a(b), .b(cin), .out(and_out_1));
23    and_gate and_2 (.a(a), .b(cin), .out(and_out_2));
24    and_gate and_3 (.a(a), .b(b), .out(and_out_3));
25
26    or_gate or_1 (.a(and_out_1), .b(and_out_2), .out(or_out_1));
27    or_gate or_2 (.a(or_out_1), .b(and_out_3), .out(cout));
28
29 endmodule
```

Types of Gate: Overview

Pre-defined Primitive Gate →



- Instantiation like a module
- **Module define (X)**
- **Minimal units for logic circuits**

Multiple : 1 Gate →


- **Input: Multiple Scalar**
- **Output: one Scalar**

 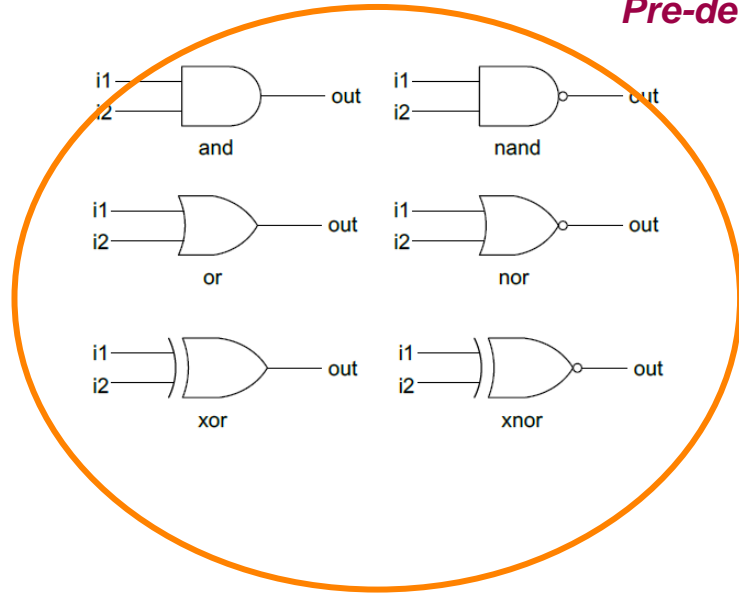1: Multiple Gate →

- **Input: One Scalar**
- **Output: Multiple Scalar**




Types of Gate: Multiple to 1 Gate

 

Gate Instance_Name (OUTPUT, INPUT1, INPUT2, ...)

```
1  wire out, i1, i2, i3;
2
3
4  // formal gate instantiation
5  and and1    (out, i1, i2);
6  nand nand1  (out, i1, i2);
7  or or1     (out, i1, i2);
8  nor nor2   (out, i1, i2);
9  xor xor2   (out, i1, i2);
10 xnor xnor2 (out, i1, i2);
11
12
13 // n-input gate
14 and and3    (out, in1, in2, in3);
15
16
17 // instantiation without name
18 or         (out, in1, in2, in3);
```

Types of Gate: 1 to Multiple

 

```
1  wire out1, out2, in;
2
3
4  // formal gate instantiation
5  buf buf1    (out1, in);
6  not not1    (out1, in);
7
8  // N-output gate
9  buf buf2    (out1, out2, in);
10
11 // instantiation without name
12 not         (out2, in);
13
```

Gate Instance_Name (OUTPUT1, OUTPUT2, ... , INPUT)



2. Module & Instance



Module: Definition

◆ Module

- ◆ Verilog에서 기본적인 설계 블록
- ◆ 상위 블록에 필요한 기능들을 제공

→ Hierarchical Structure | Design Methodology

 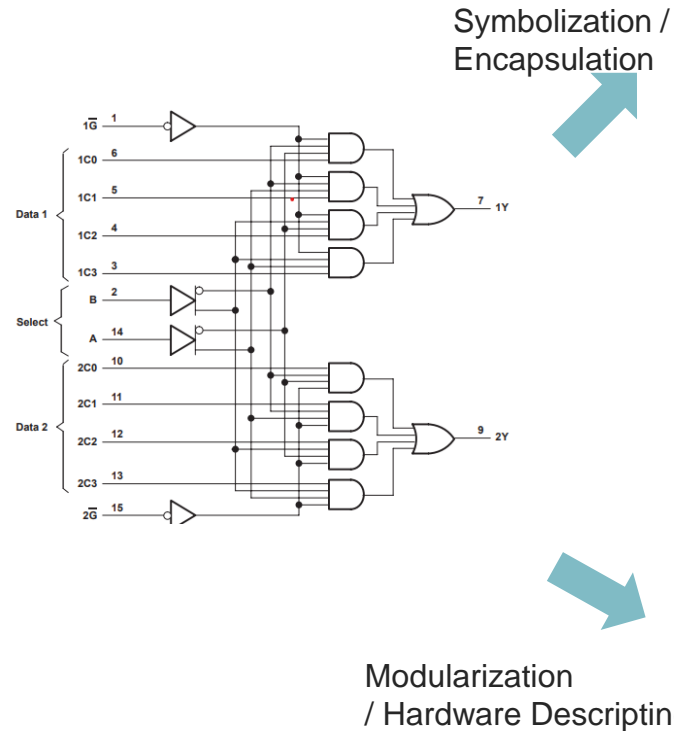- ◆ In/output의 포트 인터페이스를 제공하고 내부 상황은 은닉시킴
- abstraction / encapsulation
- ◆ 특정한 object가 만들어지는데 template을 제공함(module invocation)



Source: TI, SN54ALS153, Dual 1-of-4 Data Selectors

```
/*
Module Name: 4 X 1 multiplexor
Date Created: 28-Aug-2023
Author: William Woo
Logic: out = (~sel1 & ~sel0 & in1) | (~sel1 & sel0 & in2) |
(sel1 & ~sel0 & in3) | (sel1 & sel0 & in4);
Revision: v0.1
*/


module mux4_to_1 // 4 to 1 multiplexor
(out, // 1bit output
in1, // 1bit input1
in2, // 1bit input2
in3, // 1bit input3
in4, // 1bit input4
sel1, // 1bit selection1
sel0); // 1bit selection2

// port declaration
output wire out;
input wire in1, in2, in3, in4;
input wire sel0, sel1;

// data flow statement
assign out = (~sel1 & ~sel0 & in1) | (~sel1 & sel0 & in2) |
(sel1 & ~sel0 & in3) | (sel1 & sel0 & in4);

endmodule // finish describing the module
```

Module: component & skeleton

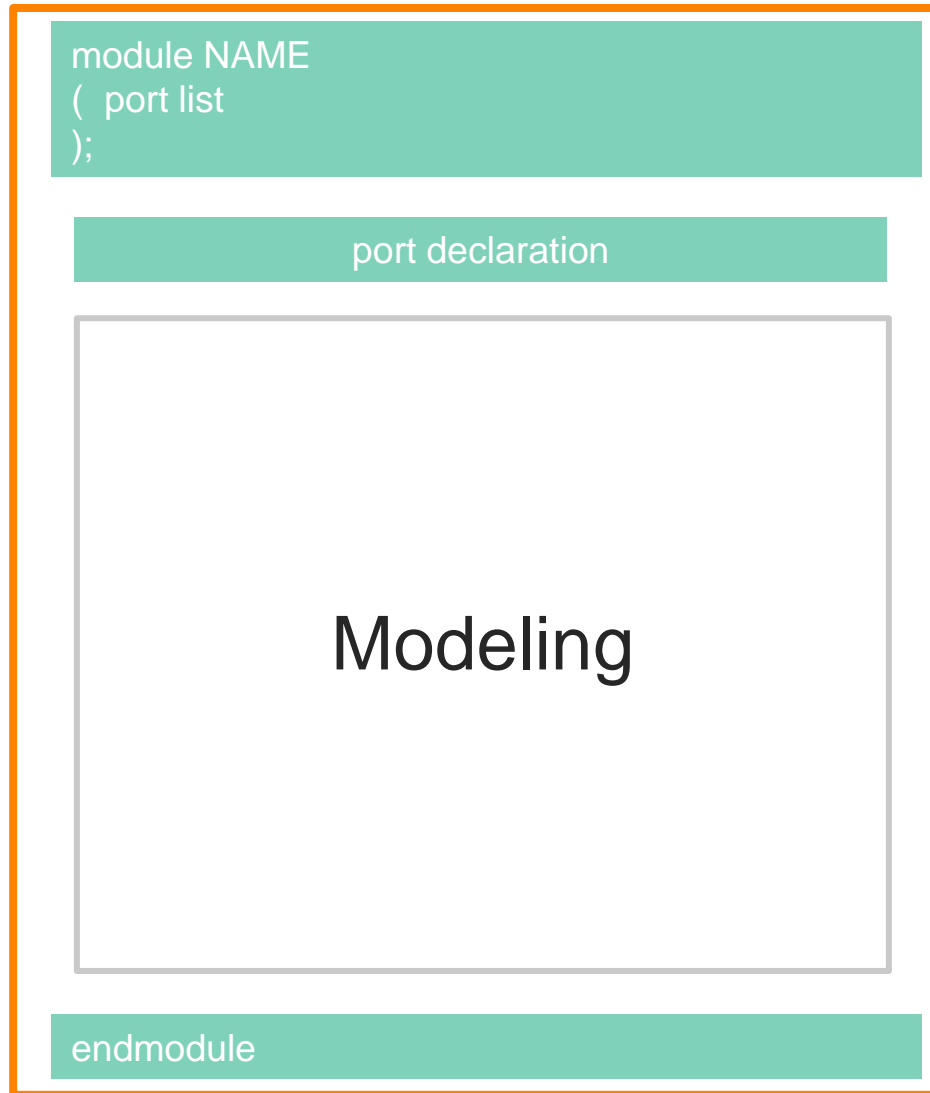


```
1  module module_name (  
2  
3      // enumerate port list  
4      in_a,  
5      in_b,  
6      out_s  
7  );  
8  
9      // port declaration  
10     input wire in_a;  
11     input wire in_b;  
12     output [3:0] out_s;  
13  
14     // Data flow statement  
15     assign =  
16  
17     // Behavioral statement  
18     // 1. always block  
19     always @(C) begin  
20  
21     end  
22  
23     // 2. initial block  
24     initial begin  
25  
26     end  
27  
28     endmodule
```


Instance: Concept

◆ Instance

- ◆ Module을 이용하여 실제로 구현된 객체(object)
- ◆ Module → 조리법(template) | Instance → 실제 음식(조립)
- ◆ Instantiation: Module이 Instance로 만들어지는 것. 상위 module에서 하위 module을 계층적으로 불러오는 것(invocation)
- ◆ 실제적인 이름, 변수, 파라미터 및 I/O Interface를 가짐

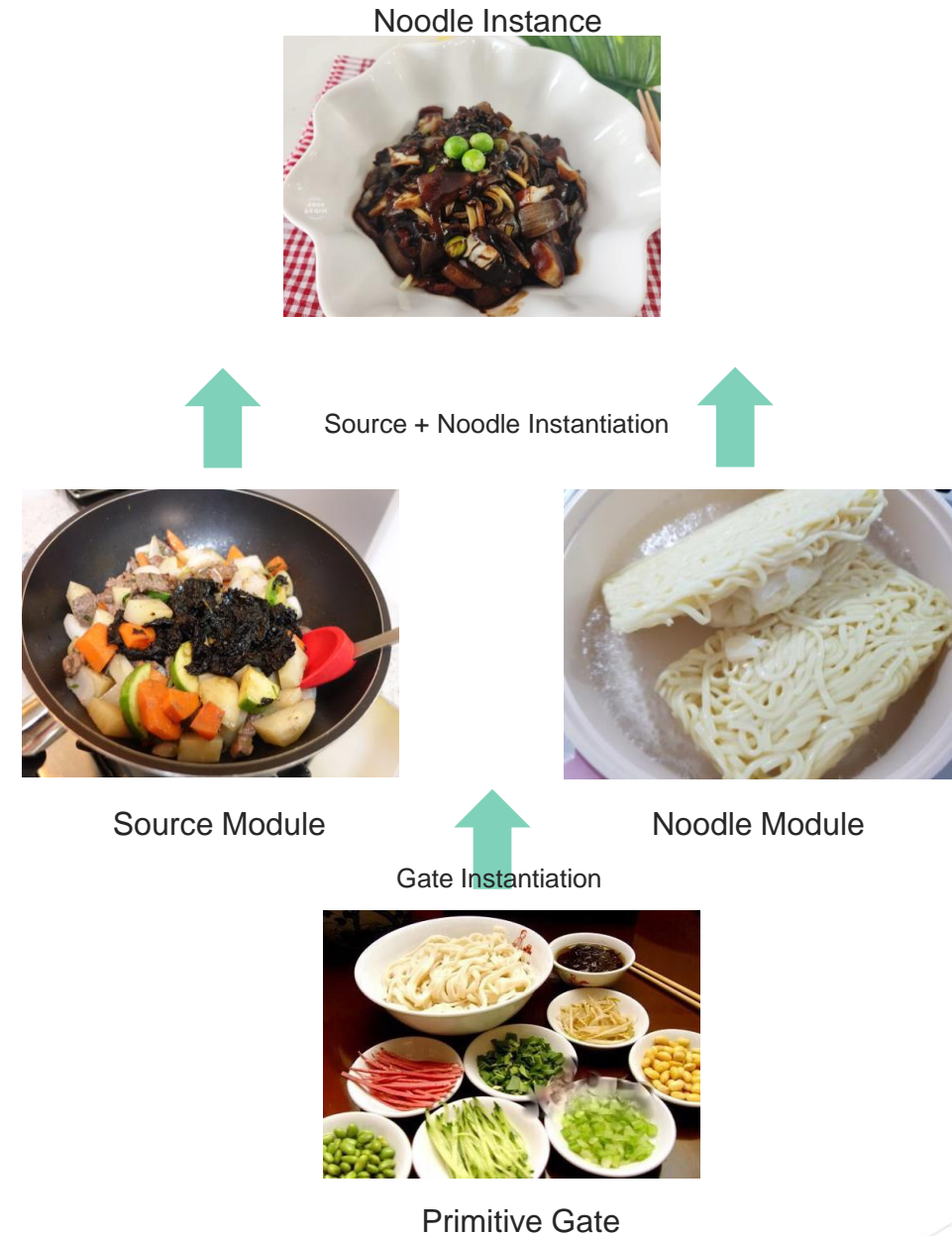


Instantiation

 



3. Testbench

Testbench

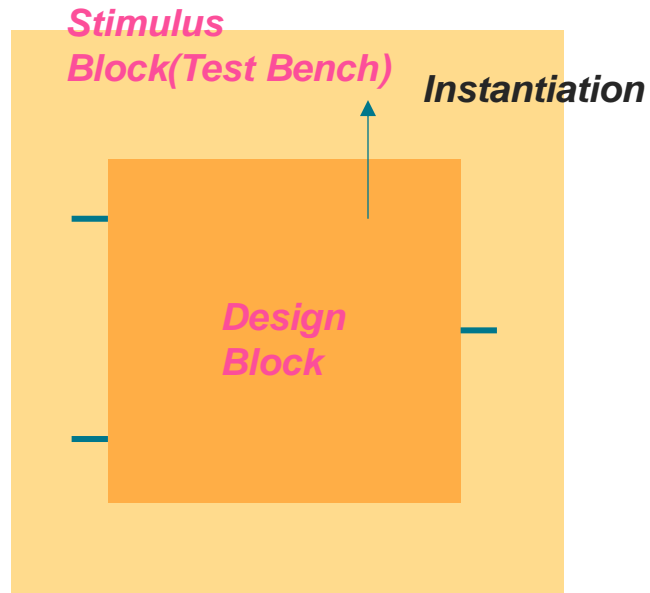

◆ Design Block

- ◆ 설계 모듈 블록
- ◆ DUT = Design Under Test

◆ Stimulus Block

- ◆ DUT를 테스트하고 로직의 결과를 확인하는 블록
- ◆ Testbench 라고도 불림

Testbench by example

```
1  module stimulus;
2  reg clk; // Input
3  reg reset; // Input
4  wire [3:0] q; // Output
5
6  ripple_carry_counter r1 (.q(q), .clk(clk), .reset(reset));
7  initial
8  clk = 1'b0; // Set clk to 0
9  always
10 #5 clk = ~clk; // Toggle clk every 5 time units
11 initial
12 begin
13 reset = 1'b1;
14 #25 reset = 1'b0;
15 #180 reset = 1'b1;
16 #10 reset = 1'b0;
17 #20 $finish;
18 end
19
20 initial
21 $monitor($time, "Output q = %d", q);
22 endmodule
```

DUT instantiation

Clock Generation

Apply stimulus

Check Result

LAB

1. [Download Datasheet](#)
2. DUT design(Gate Level)
3. Stimulus design(no clock)
4. Run simple simulation(single step)